



BUCK- BOOST CONVERTER DESIGN PROJECT REPORT

Team Member
Astik Sharma
Aditya Singh
Ishita Pandey
B. Charan teja

Roll No.
220002021
220002003
220002037
220002025

Problem Statement : Buck Boost Converter

Specifications:

Input 15 V, Output 10-20 V, Switching frequency 10 kHz, Output current 1 A. Waveforms of Switch current and diode voltage in CCM. b) Reduce switching frequency to demonstrate DCM.

Image of PWM TL 494



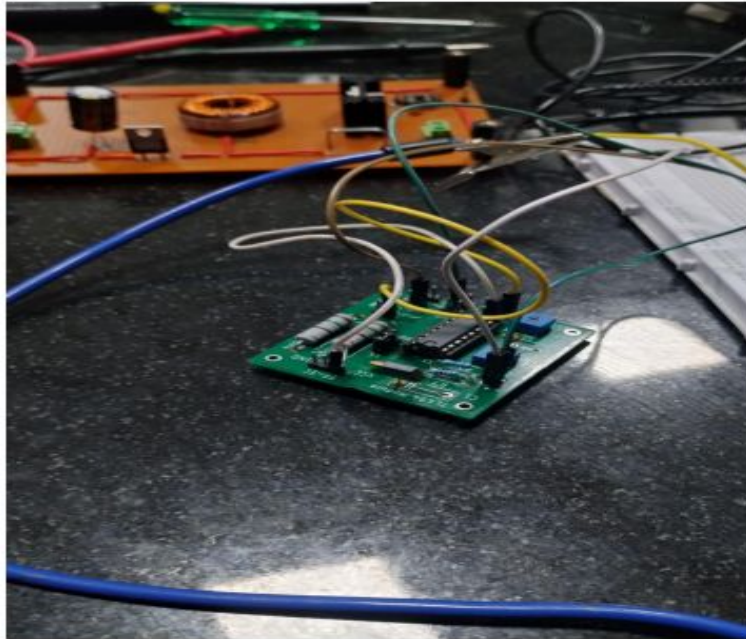


Image of PCB Board:

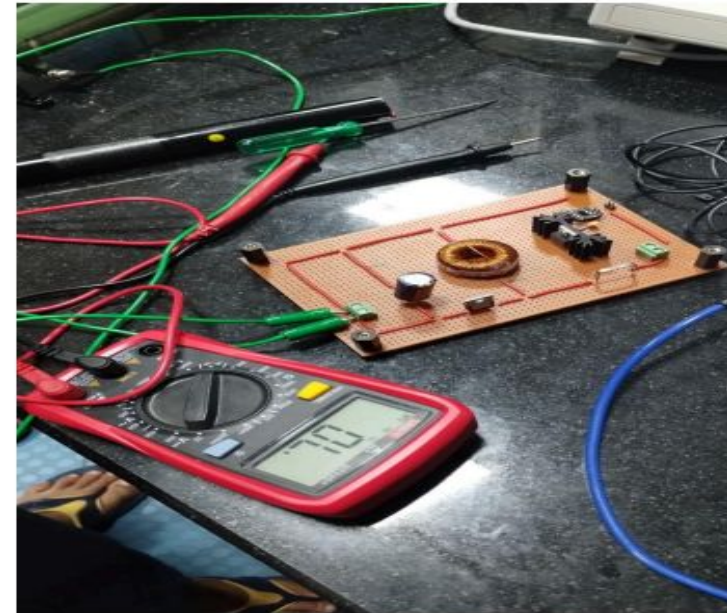


Waveforms:

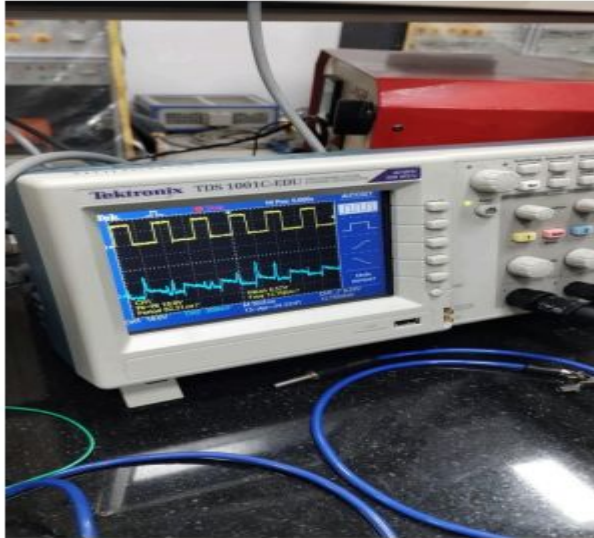

Yellow is the PWM voltage.

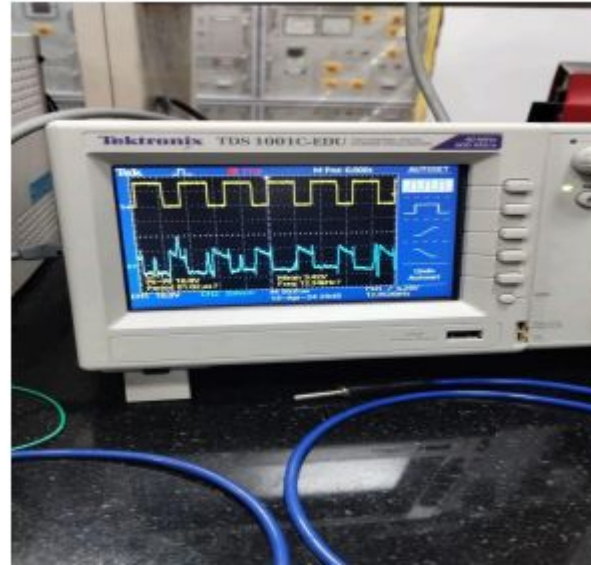Blue one is the waveform of switch current in CCM.



Blue one is the waveform of diode voltage in CCM.



[Video link](#)

Blue one is the waveform of diode voltage in BCM

Results:

Implemented buck boost converter with required specifications and demonstrated switch current waveforms in CCM and diode voltage waveforms in BCM.